


Compact Circuits for Efficient Möbius Transform

Subhadeep Banik

University of Lugano

Asian Symmetric Key Workshop on Cryptography 2023, Guangzhou

3rd December 2023

 

$$f(x+\Delta x) = \sum_{i=0}^{\infty} \frac{(\Delta x)^i}{i!} f^{(i)}(x)$$

Introduction: Solving an Equation System



- Given m eqns P_1, P_2, \dots, P_m of n variables over $\text{GF}(2)$ of max degree d .
 - Usually $m = n$, sometimes $m > n$
 - Each equation is a multivariate polynomial over $\text{GF}(2)$
 - The algebraic degree d is usually small.
 - Task: find a common root: $r \in \{0, 1\}^n$ such that $P_i(r) = 0, \forall i$.
- Problem arises in many cryptographic contexts.
 - Block ciphers with low multiplicative complexities like LowMC
 - Given single pt/ct: solving low degree polynomials.
 - Signature schemes like UOV.
 - Cryptanalysis: solving quadratic polynomials over $\text{GF}(2)$.

Truth Tables


$x_0x_1x_2$	P_0	P_1	P_2	\dots	P_m	$\bigvee P_i$
000	0	1	1		0	1
001	1	0	0		1	1
010	0	1	1		1	1
011	1	1	0		0	1
100	0	0	0		0	0
				• •		
110	0	1	0		1	1
111	0	1	1		0	1

Root=100

Möbius Transform

- Given the algebraic equation of any n -variable Boolean function, how to evaluate it over all the 2^n points of its input domain (i.e. find truth table) ?
- Given truth table of a Boolean function how to deduce its algebraic equation ?
- Answer to both the above is Möbius Transform.
- It is a linear, involutive transform that does both the above.
- Requires $n \cdot 2^{n-1}$ bit-operations.

Möbius Transform

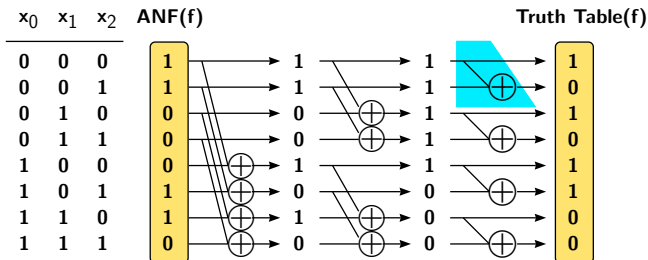


$$f = 1 + x_0x_1 + x_2 + x_0x_2$$

Figure: Möbius transform on $f = 1 \oplus x_0x_1 \oplus x_2 \oplus x_0x_2$. The blue shaded component represents one butterfly unit.

Salient Points

- Note we have lexicographical indexing.
- $t_6 = 1 \Rightarrow 6 = (110)_2 \Rightarrow$ the ANF contains the $x_0x_1 = x_0^1 \cdot x_1^1 \cdot x_2^0$ term.

Möbius Transform

 

$$f = 1 + x_0x_1 + x_2 + x_0x_2$$

Figure: Möbius transform on $f = 1 \oplus x_0x_1 \oplus x_2 \oplus x_0x_2$. The blue shaded component represents one butterfly unit.

Salient Points

- n stages and 2^{n-1} xors per stage.
- Involutive: the same operations on ANF will give back TT.

- If $\vec{v} = [v_0, v_1, \dots, v_{2^n-1}]$ be the truth-table of f (note $v_i = f(i)$).
- If $\vec{u} = [u_0, u_1, \dots, u_{2^n-1}]$ be the ANF of f .
- Then it is well known that

$$\vec{v} = M_n \cdot \vec{u}$$

- Note $M = m_{ij}$ is such that


$$m_{ij} = 1 \text{ if } j \preceq i \text{ and } 0 \text{ otherwise.}$$

- Eg $100 \preceq 101$, but $011 \not\preceq 100$ since 011 exceeds 100 in the last 2 bit-locations.

- M_n is well studied in literature: Lower triangular + Involution.
- Since $M_n = M_n^{-1}$, both $\vec{v} = M_n \cdot \vec{u}$ and $\vec{u} = M_n \cdot \vec{v}$ hold.
- Define $M_1 = \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix}$, then for all $n > 1$, we have $M_n = M_1 \otimes M_{n-1}$, where \otimes is the matrix tensor product.

$$M_3 = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 1 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 1 & 1 & 1 & 1 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 1 & 1 & 0 & 0 & 1 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 & 1 & 0 & 1 & 0 \\ 1 & 1 & 1 & 1 & 1 & 1 & 1 & 1 \end{bmatrix}$$

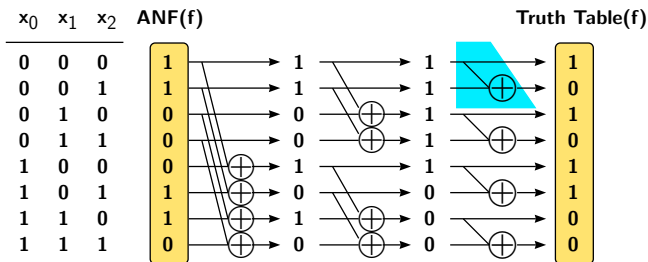Exponential circuits: The circuit Expmob1



$$f = 1 + x_0x_1 + x_2 + x_0x_2$$

Figure: Möbius transform on $f = 1 \oplus x_0x_1 \oplus x_2 \oplus x_0x_2$. The blue shaded component represents one butterfly unit.

- Huge combinatorial circuit that stacks the stages one by one.
- Calculates in one single clock cycle: $n \cdot 2^{n-1}$ xor gates.

Polynomial number of Coefficients

- ANF of Linear function: $n + 1$ coefficients.
- ANF of Quadratic function: $\binom{n}{2} + n + 1$ coefficients.
- ANF of Degree d function: $\binom{n}{\downarrow d} = \sum_{i=0}^d \binom{n}{i}$ coefficients $\in O(n^d)$.
- Challenge: With a register of size $\binom{n}{\downarrow d}$, can we compute the transform?

Take a look back

 


Figure: Round based Circuit.

- First stage $A_0 \rightarrow$ vectors A_{top} and A_{bottom} .
- A_{top} is actually ANF vector for $f(0, x_1, x_2)$ (in $n - 1$ variables!!)
- A_{bottom} is actually ANF vector for $f(1, x_1, x_2)$ (in $n - 1$ variables!!)
- Recursively apply Möbius Transform to these smaller vectors

Algorithm 1: Recursive Möbius Transform

Möbius (A_0, n, d)

Input: A_0 : The compressed ANF vector of a Boolean function f

Input: n : Number of variables, d : Algebraic degree

Output: The Truth table of f

```
/* Final step, i.e. leaf nodes of recursion tree */
if  $n=d$  then
  Use the formula  $B = M_n \cdot A_0$  to output partial truth table  $B$ .
  /* Use either Expmob1/Expmob2 to do this */
end
else
  Declare an array  $T$  of size  $\binom{n-1}{\downarrow d}$  bits.
  /* Compute the 2 operations of the butterfly layer */
1 Store 1st butterfly output i.e.  $A_{\text{top}}$  in  $T$  (requires no xors).
  Call Möbius ( $T, n-1, d$ )
2 Store 2nd butterfly output i.e.  $A_{\text{bottom}}$  in  $T$  (requires some xors).
  Call Möbius ( $T, n-1, d$ )
end
```

Recursion tree

 


Figure: Recursion tree for the Möbius Transform algorithm. The blue shaded component roughly represents one arm of the butterfly unit.

- The Tree requires Depth first Traversal
- In Software this requires context switches, every time we traverse one level down.
- Mapping to hardware non trivial.

Circuit Sketch Polymob1

 


Figure: Hardware architecture **Polymob1** for the Möbius Transform algorithm. The blue shaded part roughly represents one arm of the butterfly unit.

- Primitive attempt to map algorithm to hw: can this work ?
- Each level needs own storage of size $\binom{n-i}{\downarrow d}$
- Let us see.

Circuit Sketch Polymob1

 


Figure: Hardware architecture **Polymob1** for the Möbius Transform algorithm. The blue shaded part roughly represents one arm of the butterfly unit.

- One reg of size $\binom{n}{\downarrow d}$ for A_0 , but only one reg of size $\binom{n-1}{\downarrow d}$.
- If level 2 stores A_{top} , it must preserve this till its entire left sub-tree is executed.
- Only then overwrite to A_{bottom} .

Circuit Sketch Polymob1


 


Figure: Hardware architecture **Polymob1** for the Möbius Transform algorithm. The blue shaded part roughly represents one arm of the butterfly unit.


- Multiplexer select signals control the flow.
- 3:1 multiplexer \rightarrow Either preserve state or overwrite with $A_{\text{top/bottom}}$
- However only 2:1 mux is sufficient.

A bit of notation

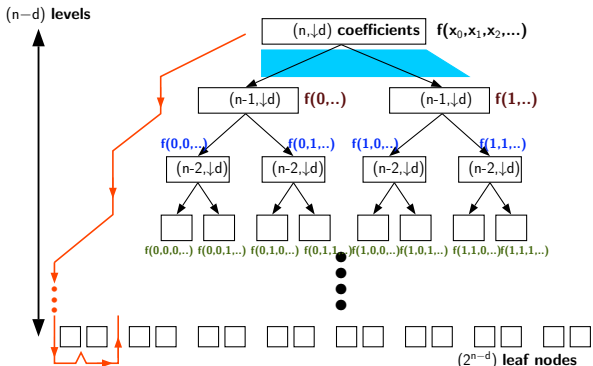


- Every level sets one bit in the function argument.

A bit of notation

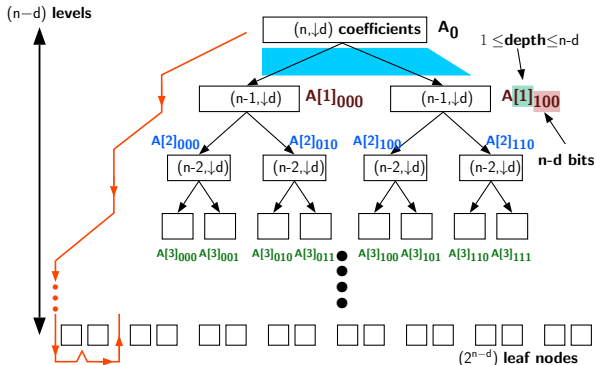


- Let us label each ANF as $A[\text{depth}]_{\text{bits}}$


A bit of notation

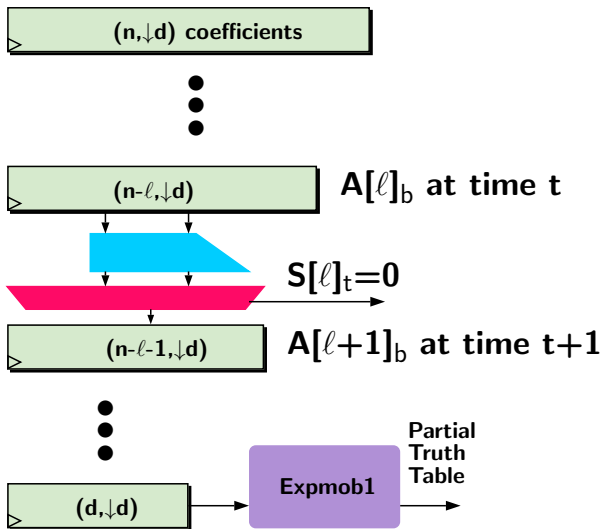


A bit of notation

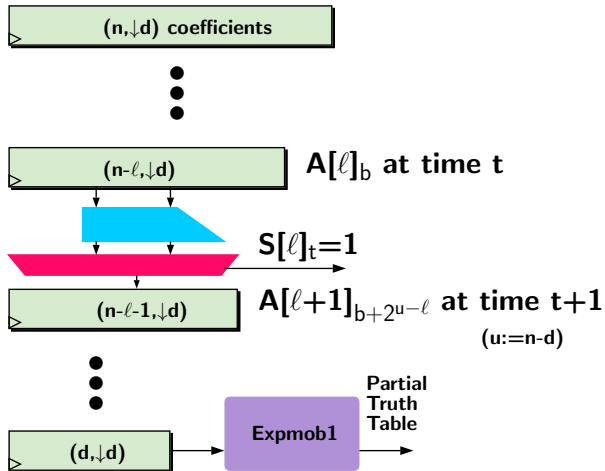


A bit of notation

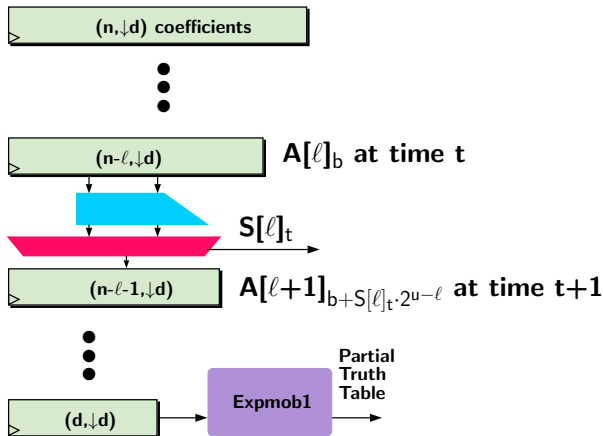


Simulation $n = 5, d = 2$

 


(a) $t=0$

 


(b) $t=1$

 


(c) $t=2$

 


(d) $t=3$

 


(e) $t=4$

 

(f) $t=5$

 

(g) $t=6$

 

(h) $t=7$

Convert to Set of Equations

t	$\ell = 0$	$\ell = 1$	$\ell = 2$	$\ell = 3$
0	0	0	0	0
1	0	$4 \cdot S[0]_0$	$2 \cdot S[1]_0$	$S[2]_0$
2	0	$4 \cdot S[0]_1$	$4 \cdot S[0]_0 + 2 \cdot S[1]_1$	$2 \cdot S[1]_0 + S[2]_1$
3	0	$4 \cdot S[0]_2$	$4 \cdot S[0]_1 + 2 \cdot S[1]_2$	$4 \cdot S[0]_0 + 2 \cdot S[1]_1 + S[2]_2$
4	0	$4 \cdot S[0]_3$	$4 \cdot S[0]_2 + 2 \cdot S[1]_3$	$4 \cdot S[0]_1 + 2 \cdot S[1]_2 + S[2]_3$
5	0	$4 \cdot S[0]_4$	$4 \cdot S[0]_3 + 2 \cdot S[1]_4$	$4 \cdot S[0]_2 + 2 \cdot S[1]_3 + S[2]_4$
6	0	$4 \cdot S[0]_5$	$4 \cdot S[0]_4 + 2 \cdot S[1]_5$	$4 \cdot S[0]_3 + 2 \cdot S[1]_4 + S[2]_5$
7	0	$4 \cdot S[0]_6$	$4 \cdot S[0]_5 + 2 \cdot S[1]_6$	$4 \cdot S[0]_4 + 2 \cdot S[1]_5 + S[2]_6$

- Left Column needs to be $0, 1, 2, 3, \dots, 7$
- Solve the integer equation system: look for solutions in $\{0, 1\}$

General Case ($u := n - d$)

$$\begin{array}{cccccccc}
 & & & & & & 2 \cdot S[u-2]_0 & + S[u-1]_0 & = 1 \\
 & & & & & & & + S[u-1]_1 & = 2 \\
 & & & & & & & & \vdots \\
 & & & & & & & + S[u-1]_i & = i + 1 \\
 & & & & & & & & \vdots \\
 2^{u-1} \cdot S[0]_0 & + 2^{u-2} \cdot S[1]_1 & + \cdots + 2^i \cdot S[j]_j & + \cdots & + S[u-1]_{u-1} & = u \\
 2^{u-1} \cdot S[0]_1 & + 2^{u-2} \cdot S[1]_2 & + \cdots + 2^i \cdot S[j]_{j+1} & + \cdots & + S[u-1]_u & = u + 1 \\
 & & & & & & & & \vdots \\
 2^{u-1} \cdot S[0]_{2^u - u - 1} & + 2^{u-2} \cdot S[1]_{2^u - u} & + \cdots + 2^i \cdot S[j]_{-i + 2^u - 2} & + \cdots & + S[u-1]_{2^u - 2} & = 2^u - 1
 \end{array}$$

- Look at the i -th column shaded in green (note $j = u - 1 - i$)
- $S[j]_t$ is the $i + 1$ -th lsb of $(i + 1), (i + 2), \dots$, i.e. the $(i + 1)$ -th lsb of $t + i + 1$.

General Case ($u := n - d$)

$$\begin{array}{rcccccccc}
 & & & & & & & 2 \cdot S[u-2]_0 & + \frac{S[u-1]_0}{S[u-1]_1} & = 1 \\
 & & & & & & & & & = 2 \\
 & & & & & & & & & \vdots \\
 & & & & & & & & + S[u-1]_i & = i + 1 \\
 & & & & & & & & & \vdots \\
 2^{u-1} \cdot S[0]_0 & + 2^{u-2} \cdot S[1]_1 & + \cdots + 2^i \cdot S[j]_j & + \cdots & + S[u-1]_{u-1} & = u \\
 2^{u-1} \cdot S[0]_1 & + 2^{u-2} \cdot S[1]_2 & + \cdots + 2^i \cdot S[j]_{j+1} & + \cdots & + S[u-1]_u & = u + 1 \\
 & & & & & \vdots \\
 2^{u-1} \cdot S[0]_{2^u - u - 1} & + 2^{u-2} \cdot S[1]_{2^u - u} & + \cdots + 2^i \cdot S[j]_{-i + 2^u - 2} & + \cdots & + S[u-1]_{2^u - 2} & = 2^u - 1 \\
 & & & & & \vdots
 \end{array}$$

- A u -bit decimal up-counter for the variable t .
- A series of u incrementers to generate $t + 1, t + 2, \dots, t + u$.

Circuit is implementable in logarithmic depth

 


Figure: Visual representation of the addition $t + i + 1$

- Having the whole incrementer circuit is unnecessary.
- We are only interested in $(i + 1)$ -th lsb of $t + i + 1$.
- The expression is $x_i \oplus z_s \prod_{k=n_s+1}^{i-1} x_k$.
- Can be implemented using $2 \log_2 u$ depth.

 


Figure: Hardware Solver **Polysolve1**

- After OR-ing, Priority Encoder gives the location of 1st 0 in the table.
- The solver will extract one root per partial truth table.
- Note large critical path !!

Polysolve2


 


Figure: Hardware Solver **Polysolve2**

- Pipelining reduces the length of critical path.

Polysolve3

 

Example

If $d = 4$, and the **OR** of the truth tables is $T_0 = 1011\ 1111\ 1111\ 0111$

- At $\tau = 0$ Penc outputs 0001
- Decoder op $D_0 = 0100\ 0000\ 0000\ 0000$
- $T_1 = T_0 \vee D_0 = 1111\ 1111\ 1111\ 0111$
- $HW(T_1) = HW(T_0) + 1$, and is written back to **Reg2**.

- At $\tau = 1$ Penc outputs next root 1100
- We have $D_1 = 0000\ 0000\ 0000\ 1000$.
- $T_2 = T_1 \vee D_1 = 1111\ 1111\ 1111\ 1111$ which is now the all one string.


Wasteful Computation

- Suppose we have 50 equations in 50 variables.
 - The common solution of 1st 10 equations is 100.
 - Evaluating Möbius Transform for the remaining equations \Rightarrow Evaluating 40 equations at 2^{50} points each.
 - Evaluating 40 equations at 10 points is sufficient !!!!
- We found energy efficient solution for this.
- The idea is to filter any common root of first 10 eqns using Dot-product circuit.

Circuit components

- Root expander: $RE(n, d): \{0, 1\}^n \rightarrow \{0, 1\}^{\binom{n}{\downarrow d}}$.
 - Eg. $RE(4, 3)$ over the vector $(x_0, x_1, x_2, x_3) = (1, 0, 1, 1)$
 - const value = 1, $x_0x_1 = 0$, $x_0x_2 = 1$, $x_0x_3 = 1$, $x_1x_2 = 0$, $x_1x_3 = 0$,
 $x_2x_3 = 1$, $x_0x_1x_2 = 0$, $x_0x_1x_3 = 0$, $x_0x_2x_3 = 1$, $x_1x_2x_3 = 0$.
 - The expanded root $\mathbf{r} = 1111\ 0001\ 110$
 - Total hardware overhead is $\binom{n}{\downarrow d} - n$ **AND** gates.
- Dot-Product: Eg $f = 1 \oplus x_0 \oplus x_2 \oplus x_0x_1 \oplus x_2x_3$.
 - Vector Description $\mathbf{v} = 1011\ 0001\ 001$.
 - The dot-product $\mathbf{r} \cdot \mathbf{v} = 0$, equals $f(\mathbf{r})$.
 - $\binom{n}{\downarrow d}$ **AND** gates and $\binom{n}{\downarrow d} - 1$ **XOR**

Circuit

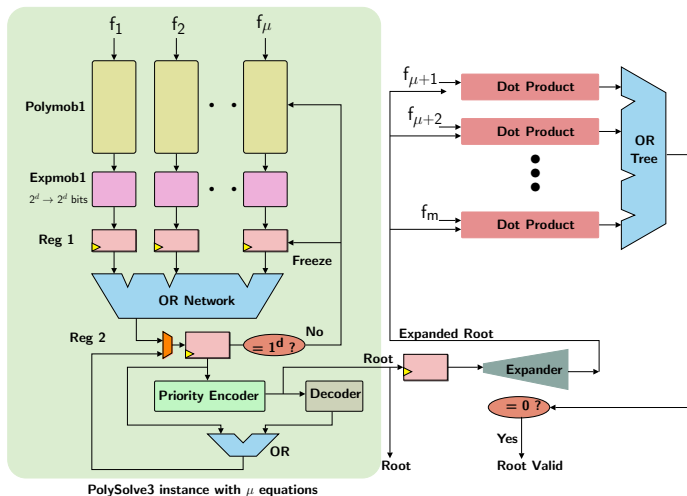

Energy

 


Figure: Energy consumption for varying μ for $n = m = 20$. The colored dashed lines show the energy consumed in the **Polysolve3** circuit for the corresponding equation systems.

 


Figure: SAKURA-X

Proof of Concept

- SAKURA-X mainly built for side-channel experiments, limited computational power.
- We could solve quadratic equations of upto 50 variables in 8 hours.
- TODO → Implement on an FPGA cluster and solve upto 100 variables.

Conclusion



- Given m equations in n variables over $GF(2)$.
- Asymptotically, all the solutions can be found using a circuit of area $\propto m \cdot n^{d+2}$.
- This is not energy-efficient however: Möbius Transform does a lot of redundant computations.
- Circuit for energy efficiency also proposed.

THANK YOU